

Ohm's Law Problems

1. (a) What is the voltage across the resistor if the two cells are each 1.5 V in Figure 1?

(b) If a current of 0.10 A is measured at point *a*, what is the resistance of the resistor? What is the current at *b*?

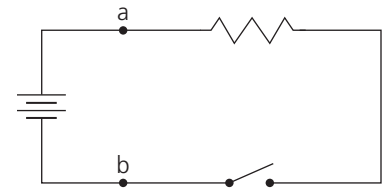



Figure 1

2. If a toaster has a resistance of $220\ \Omega$, how much current will it draw from a 110 V outlet?
3. A calculator runs on two 6.0 V dry cells connected in parallel. If the calculator draws 0.001 A, how many milliamps (mA) does it draw? What is the effective resistance of the calculator?
4. A resistor has a value of $100\ \Omega$. If a current of 5 mA passes through it, what is the applied voltage?
5. A resistance has a voltage of 10 mV (millivolts) applied to it. The current through the resistance is 0.5 mA. What is the value of the resistance?
6. A hair dryer uses a current of 10 A when plugged into a 120 V outlet. What is the resistance of the hair dryer?


Ohm's Law Problems (continued)

7. Draw circuit diagrams for the following circuits. The resistance of the filament in each light bulb is 8.2Ω and the voltage of each cell is 1.5 V . Determine the current through the bulbs when the switch is closed in each circuit.


a)

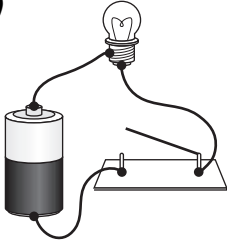

b)

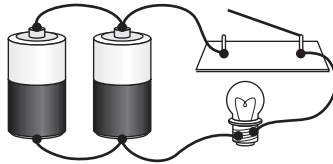

c)

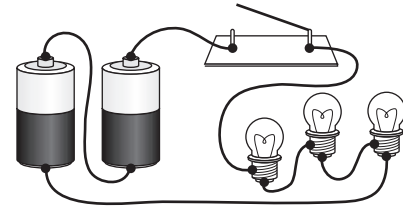

8. Complete the following chart.

Voltage (V)	Current (A or mA)	Resistance (Ω)
_____	5 A	200
250	_____ A	500
4.5	900 mA	_____
_____	250 mA	4.0
4.0	_____ A	2.0
12	400 mA	_____
15	_____ A	30
9	_____ mA	180
12	600 mA	_____
_____	50 mA	1.0
6	_____ A	2
12	750 mA	_____
3.0	_____ mA	100
_____	200 mA	250
10	_____ A	50